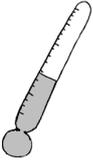
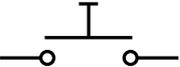
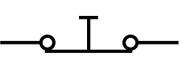
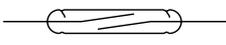
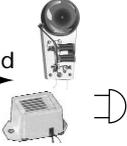
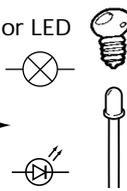
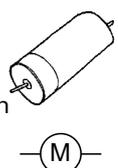
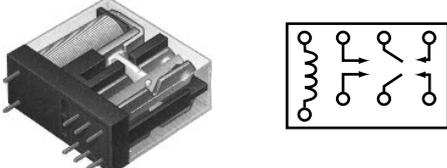
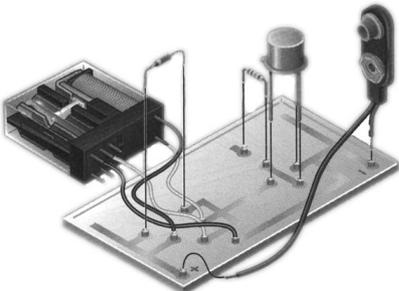
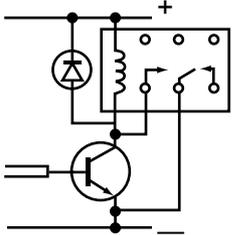
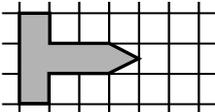
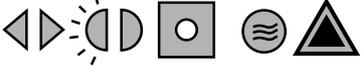


Sensing with Electronics Chooser Chart

When designing the INPUT ask yourself: <i>What does the system need to detect?</i>				
a change in temperature 	a change in light level 	moisture 	movement 	
What sensors could I use for this detecting?				
light-dependant resistor  light → [light sensor] → electronic signal	thermistors  temperature → [temperature sensor] → electronic signal	moisture sensor  moisture → [moisture sensor] → electronic signal		
What switches could I use for this detecting?				
push-to-make 	push-to-break 	change-over 	reed 	tilt 
When designing the PROCESSOR ask yourself: <i>Do I need to increase the signal from the sensor or switch?</i>				
no – go to <i>When designing the output</i>		yes – use a single transistor or a Darlington pair 		
When designing the OUTPUT ask yourself: <i>What does the output need to do?</i>				
make a sound – use a buzzer or bell electronic signal → [buzzer or bell] → sound 	make a light – use a bulb or LED electronic signal → [lamp or LED] → light 	make a movement – use a motor electronic signal → [motor] → motion 		
Is the output a high-current device?				
no – connect directly to processor		yes – use a relay 		
Does the system need to keep the output on after the input has ceased?				
yes – use a relay and latch 				

When designing the PRODUCT CASING AND STYLE ask yourself:		
<i>What overall shape and size would be suitable?</i>	large enough to take the contents but small enough for hand-held use – try modelling for fit	
<i>What does the user like?</i>	try using an image board	
<i>How can I get an appearance that fits in with where it will be used?</i>	try out some ideas against the image board	
When designing the USER INTERFACE ask yourself:		
<i>What switches, other controls or indicator lights will the user need?</i>	try an imaginary user trip	
<i>How can I make the layout of the controls look easy to understand?</i>	try modelling with a plan	
<i>How can I make it clear what each switch or indicator light is for?</i>	try labelling with signs or symbols	
<i>How can I position switches and other controls so they are easy to operate?</i>	try ergonomic modelling	

What if it doesn't work

Ask yourself these questions:

Is the battery working and is it the right way round?

Check to be sure.

Is everything in the right place?

Check to be sure.

Are all the components the right way round?

Check the transistors, LEDs and diodes.



Are there any loose connections?

Look carefully to check.

Are there any dry joints?

Check carefully.

Are there any cracks in the copper tracks of the PCB?

Look carefully to check.